

# Transient and Frequency Analysis of various Analog, Op-Amp and Mixed Signal Circuits using LTSpice

## Introduction: -


The project aims to simulate, analyse and understand the behaviour of various analog circuits by utilising transient and frequency analysis on LTSpice.

Following are a few circuit simulations.

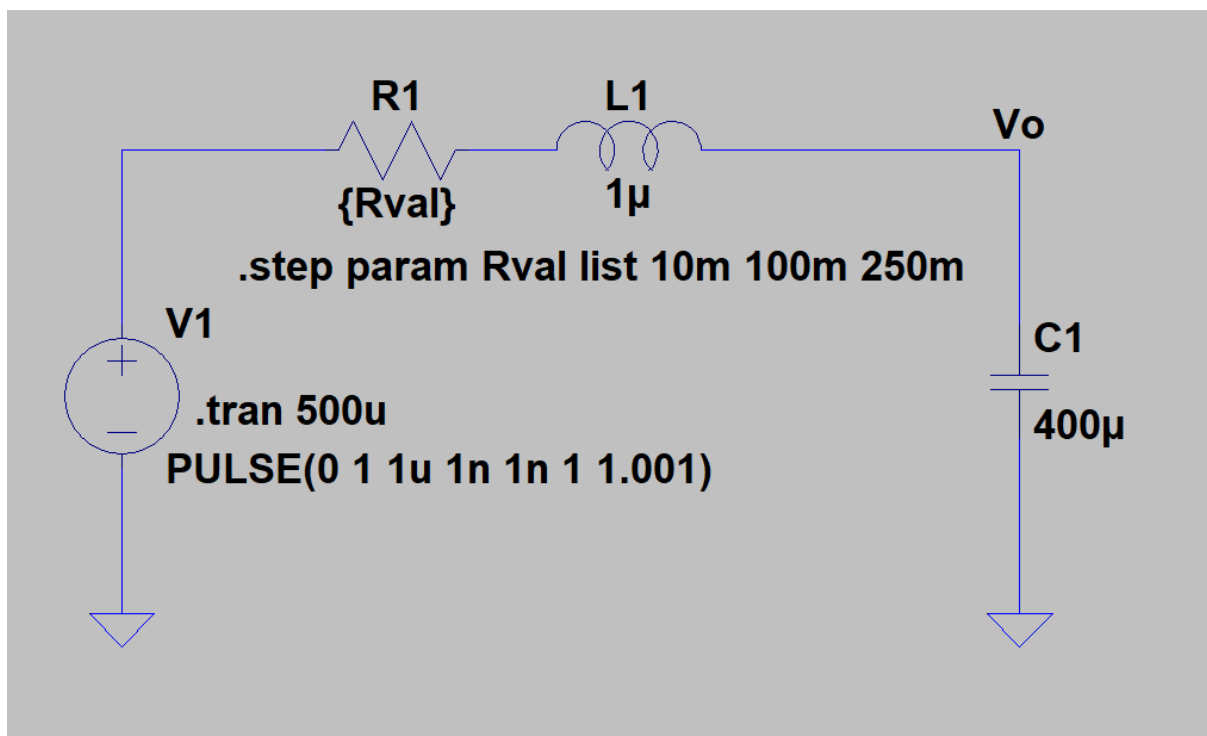
## Transient analysis of series RLC circuit: -

For  $C = 400\mu\text{F}$  and  $L = 1\mu\text{H}$ , we get the value of  $R = 100\text{ m-}\Omega$  to be the condition for critically damped (from  $R^2 = 4(L/C)$ ). Any value of  $R$  less than this would render the circuit to operate in an under-damped condition while the value of  $R$  greater than this would make it operate in an over-damped condition.

Attached are the circuit along with simulation parameters and the waveform.




*Schematic for transient analysis*

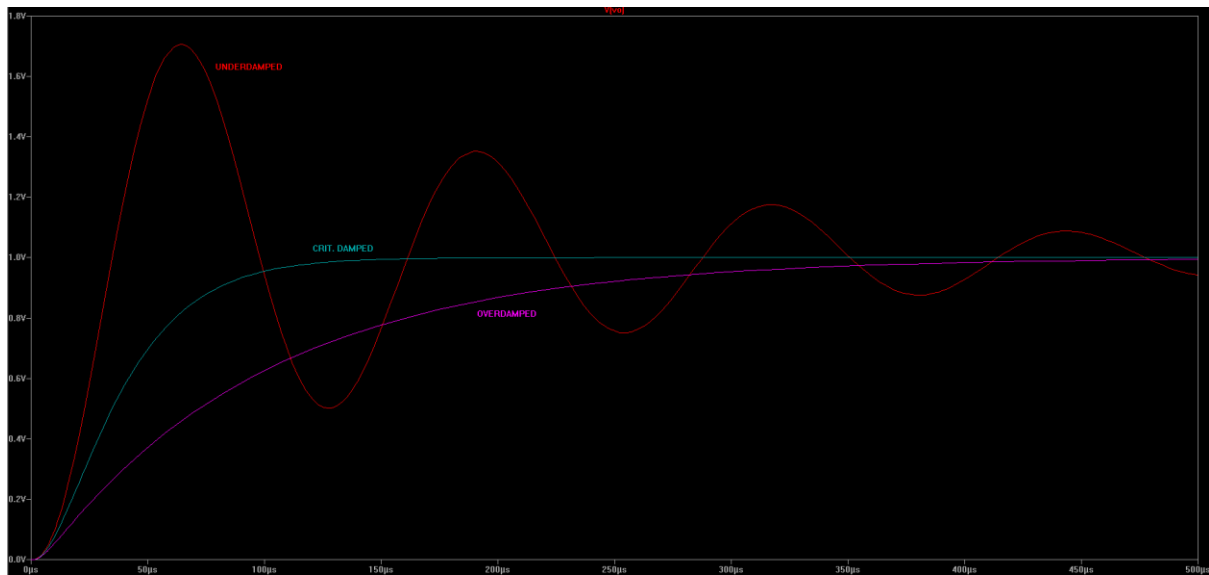


*Transient analysis plot*
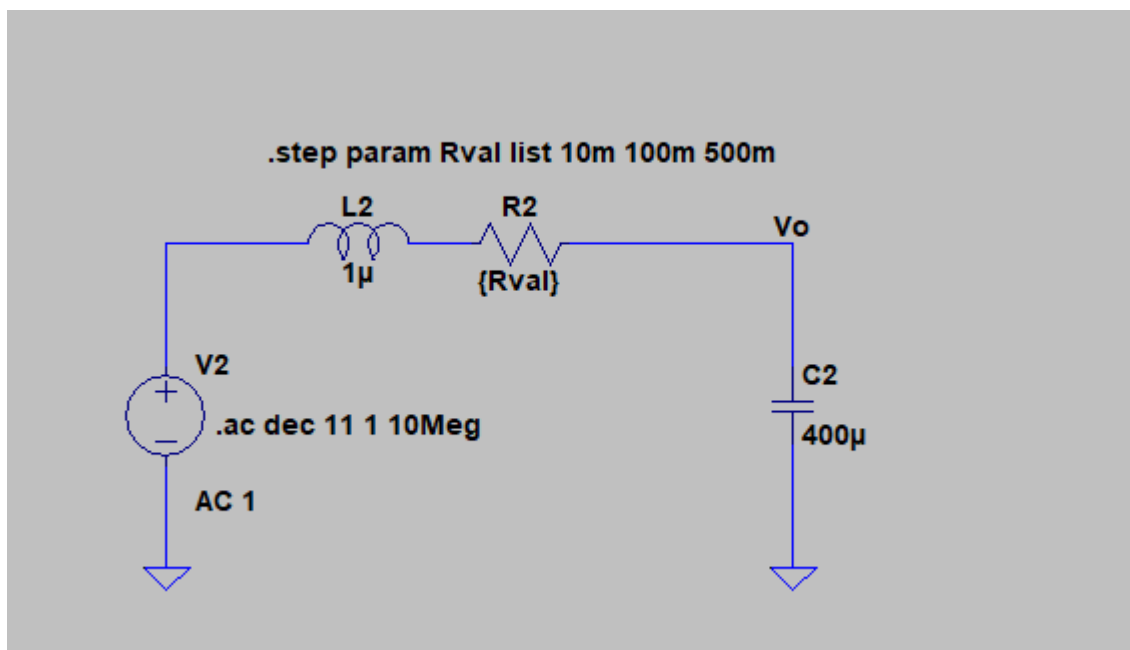
## Frequency Analysis of Series LRC Circuit: -



*Schematic for AC analysis*

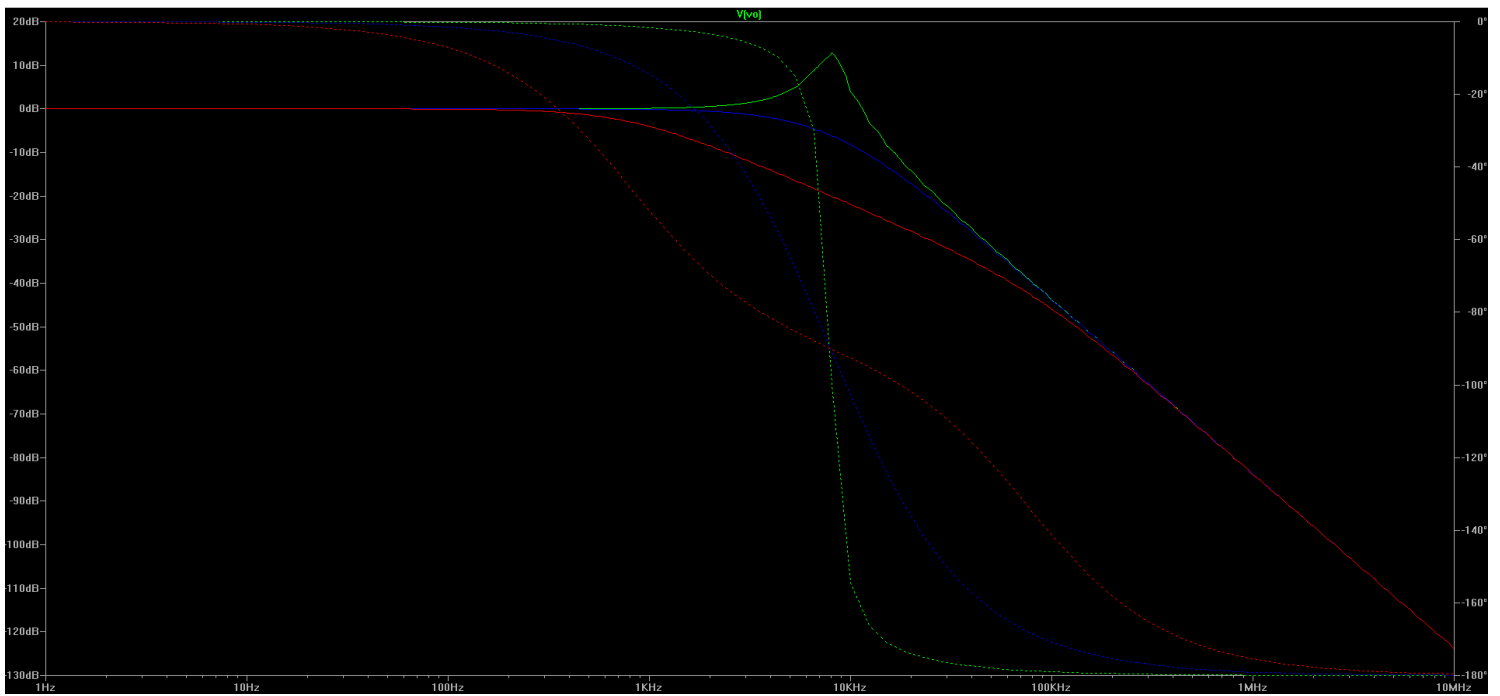
I have used a similar circuit (LRC instead of RLC), performed AC analysis using decade sweep from 1Hz to 10 MegHz, and parameter sweeps to represent 3 cases for showing bode plots of over, under and critically damped cases.




Bode plots
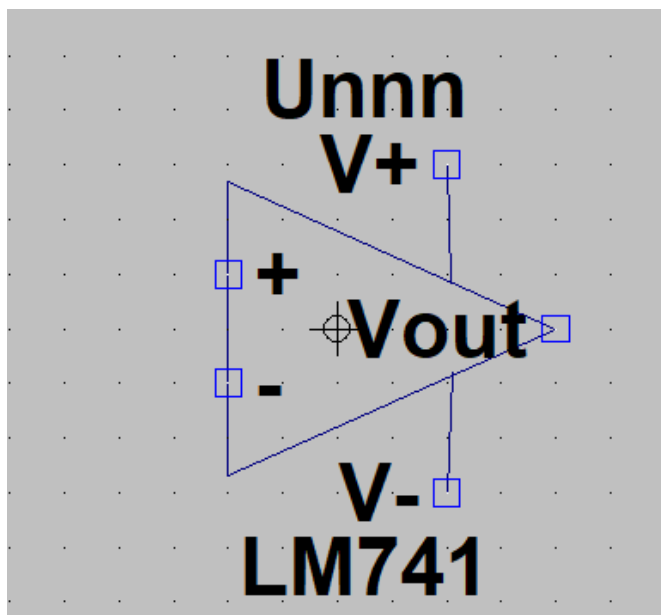
## Inverting Op-Amp: -


I have utilised the LM741 Op-Amp here. Since it is not available in the standard LTSpice library I had to download its file from the TI website and restructure the schematic making it visually easier to understand.




Created schematic for LM741

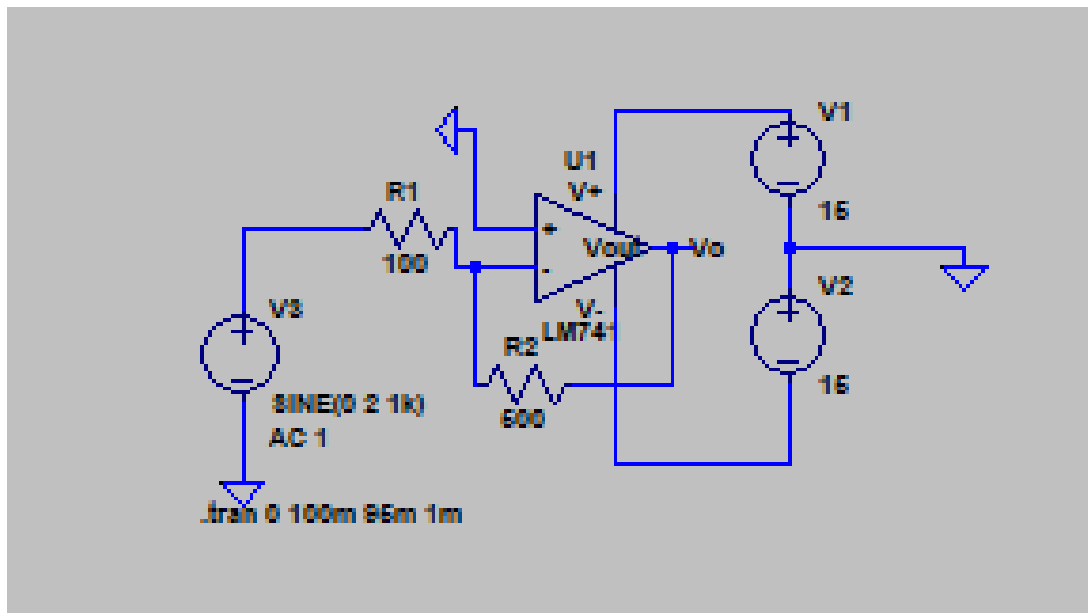


*Schematic for inverting Op-Amp*

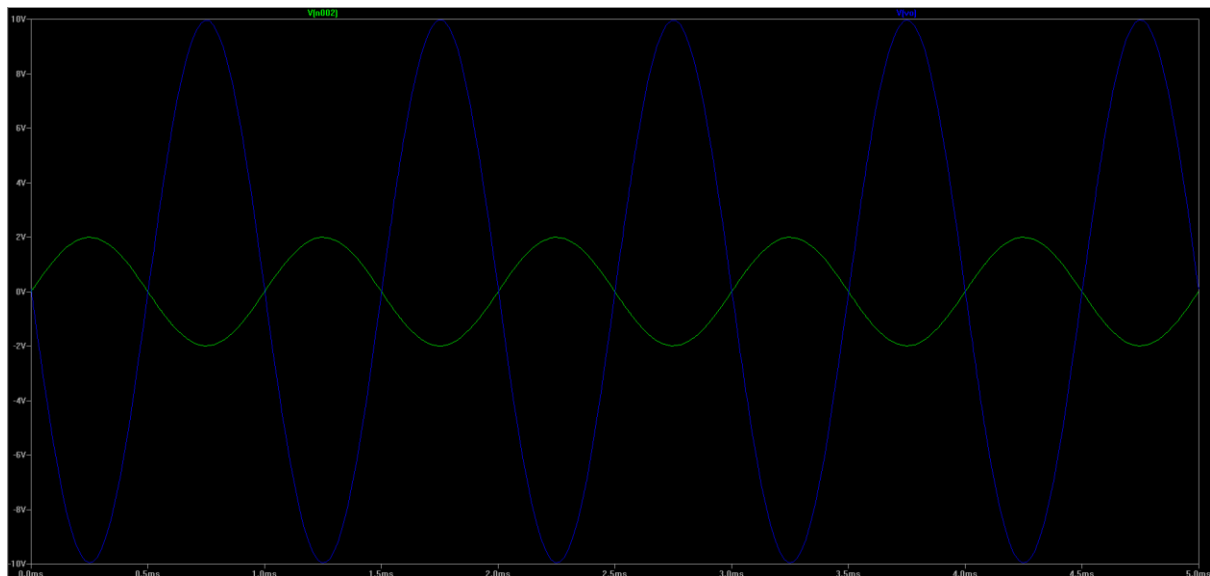

*Waveform for inverting Op-Amp*

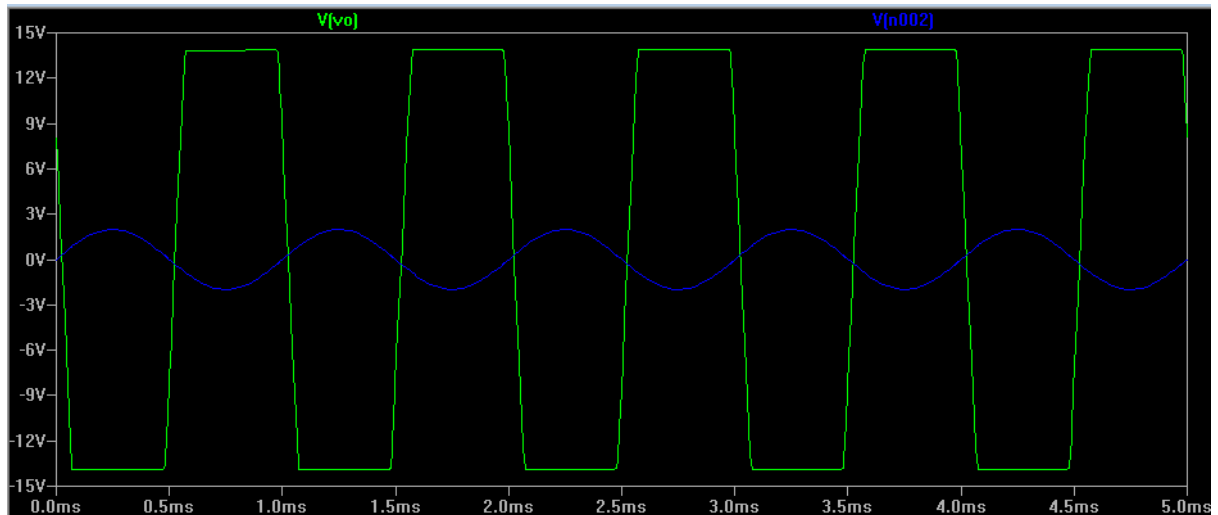


*Clipping when gain is excess*

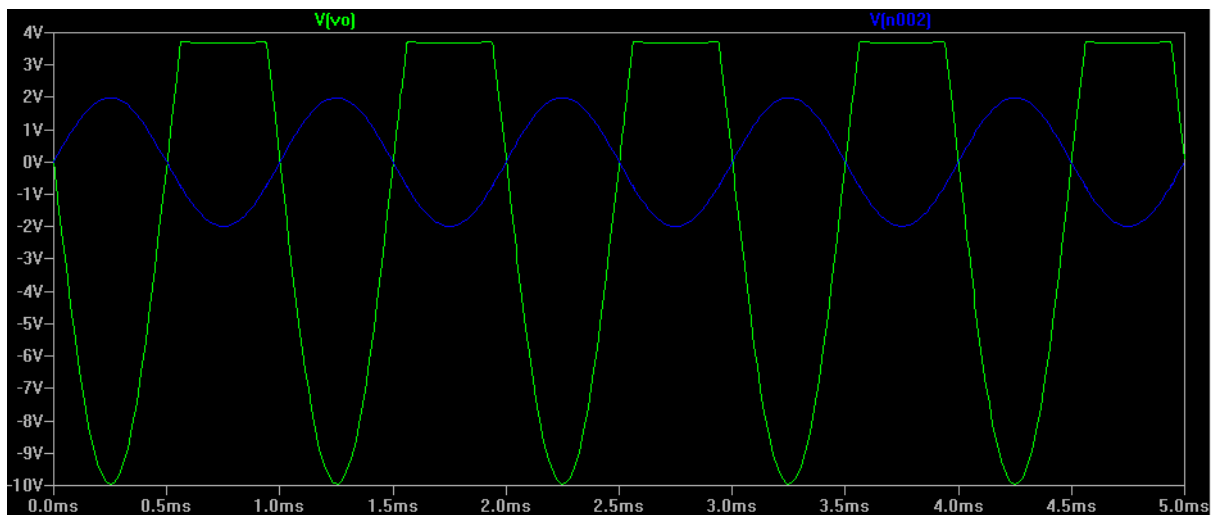


*Positive clipping when Vcc+ is reduced*

## Differentiator Op-Amp: -

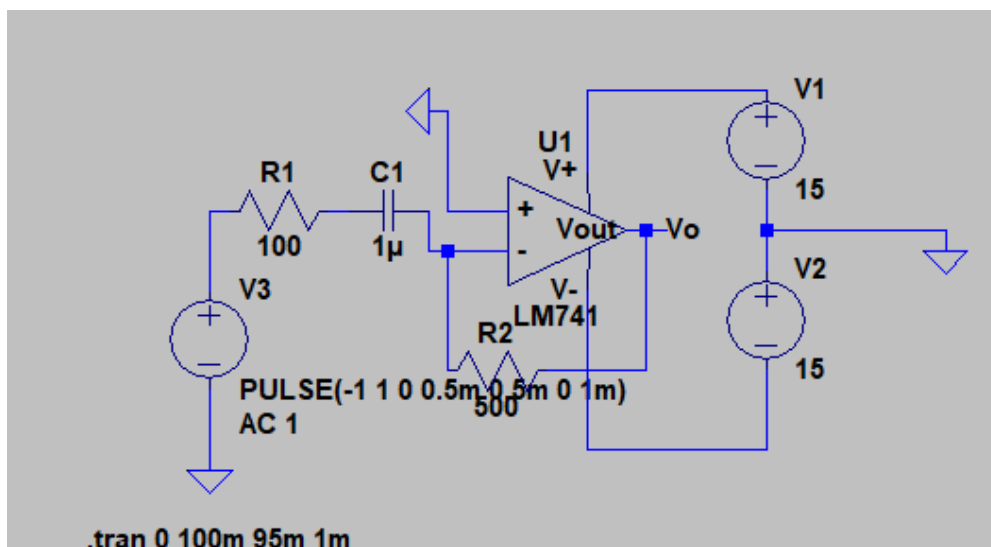

*Differentiator Op-Amp Schematic*

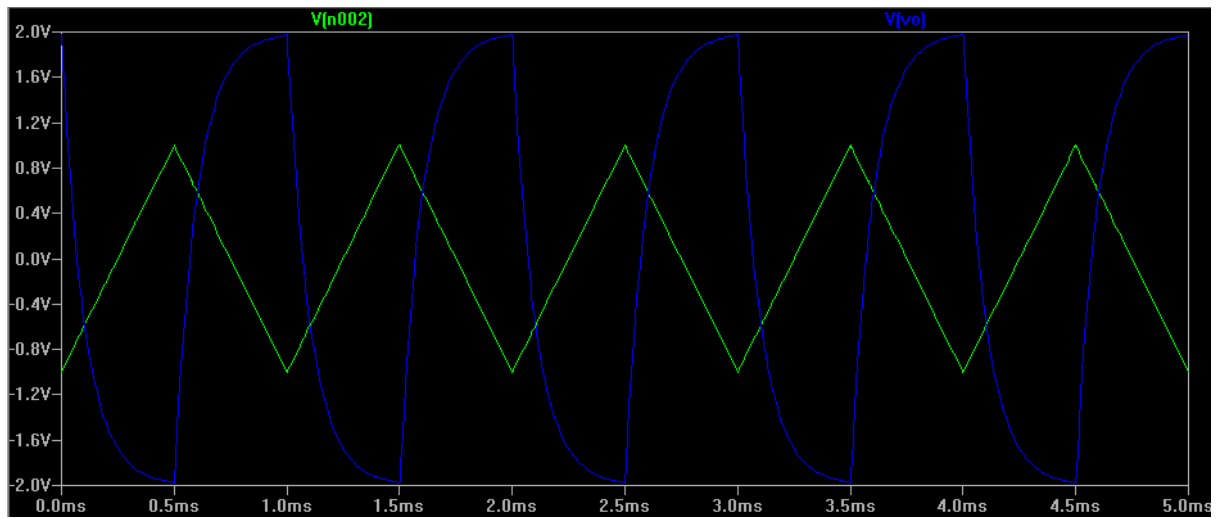

Waveform